

<b>Name :</b>	<b>Ehab Mostafa Farghly</b>
<b>Track :</b>	<b>DIGITAL IC Design</b>

## **I. Overview:**

The RISC-V processor architecture is like a set of tools that people can use to design computer processors. These processors can be made to work well for different tasks and can be adjusted to fit specific needs. This architecture is open to anyone, meaning people can look at it, change it, and use it freely. It's designed to be easy to work with and can be customized to make processors that are both simple and powerful.

RISC-V offers various ways to make processors, including:

**Single Cycle:** In a single-cycle architecture, each instruction takes a single clock cycle to complete. While conceptually simple, it's not highly efficient for modern processors due to potentially long cycle times for complex instructions.

**Multicycle:** The multicycle architecture divides the instruction execution into multiple stages, such as instruction fetch, decode, execute, memory access, and write-back. Each stage takes a cycle, allowing for more efficient use of resources.

**Pipelined:** Pipelining breaks down instruction execution into a series of stages, with different instructions at various stages simultaneously. This enables higher throughput and improved performance as long as hazards (data dependencies, control dependencies) are managed effectively.

## RISC-V (Single Cycle)

RISC-V offers various types of operations, including:

- R-type: like ADD,SUB,AND,SLT,SLL.....
- I-type: like lw,addi.....
- B-type:like beq,bnq,...
- S-type:like sw,.....
- J-type:Jalr,Jal,.....

31	30	25	24	21	20	19	15	14	12	11	8	7	6	0	
funct7				rs2			rs1		funct3		rd			opcode	R-type
imm[11:0]						rs1		funct3		rd			opcode	I-type	
imm[11:5]				rs2			rs1		funct3		imm[4:0]			opcode	S-type
imm[12]	imm[10:5]			rs2			rs1		funct3		imm[4:1]	imm[11]	opcode	B-type	
imm[31:12]										rd			opcode	U-type	
imm[20]	imm[10:1]				imm[11]		imm[19:12]			rd			opcode	J-type	


Figure 1 Different Types of operation on RISC-V

## II. Architecture:

In this short paper, we will create and explain the RISC-V Single Cycle processor design in simple steps.

Our design consists of 2 basis Block:

- **Datapath:** The Datapath operates on words of data. It contains structures such as memories, registers, ALUs, and multiplexers. We are implementing the 32-bit RISC-V (RV32I) architecture, so we use a 32-bit Datapath.
- **Controller:** The control unit receives the current instruction from the Datapath and tells the Datapath how to execute that instruction. Specifically, the control unit produces multiplexer select, register enable, and memory write signals to control the operation of the Datapath.

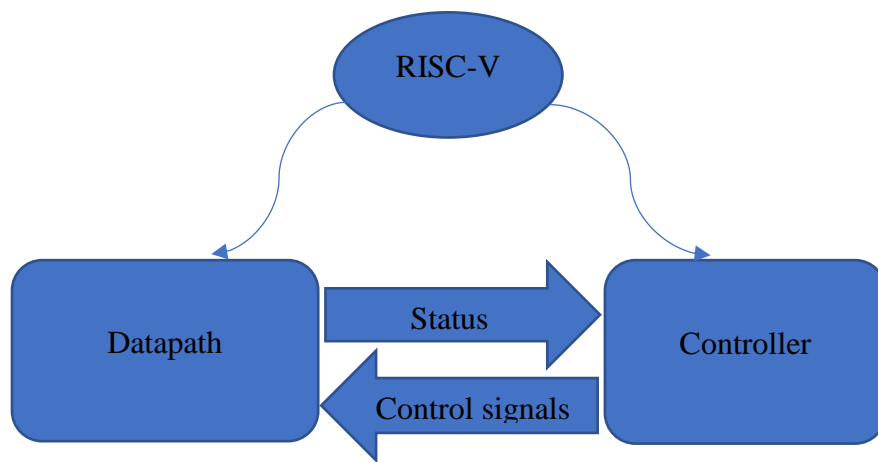

### Datapath Structure:

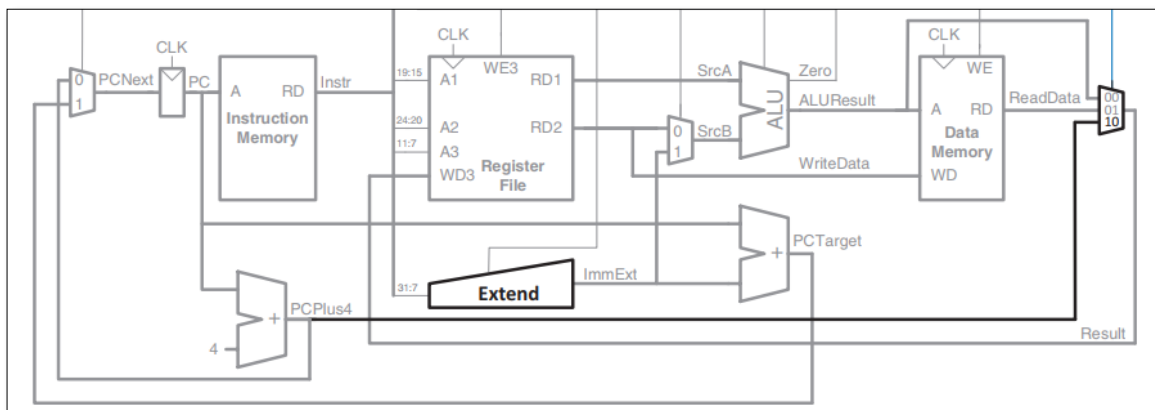


Figure 2 Datapath Structure

## RISC-V (Single Cycle)

Datapath Architecture consist of:

- I. **PC (Program Counter):** keeps track of the memory address of the current instruction being executed. that indicates where the processor is in the program's sequence of instructions.
- II. **Instruction Memory:** that holds all the instructions for a program. Each instruction tells the processor what specific task to perform. The Instruction Memory is responsible for storing these instructions in a specific order.
- III. **Register File:** It serves as a rapid-access storage space for temporary data, allowing the processor to swiftly perform calculations and operations without constantly fetching data from slower main memory.
- IV. **Data Memory:** Acts as a storage hub for larger and longer-term data storage in a processor's operation. It enables the efficient exchange of data between the processor and memory.
- V. **ALU:** Used in executing arithmetic and logic instructions. It takes data from the Register File, performs the required operation, and provides the result to be stored back in registers or used for further computations. processor and memory.
- VI. **Sign Extension:** extends a smaller binary number to a larger size, we apply it in immediate and sign extension differ respect to type operation.
- VII. **MUXS:** Used in some locations
  - Instruction Fetch: Mux determine whether the next instruction comes from the Instruction Memory, based on control signals. This choice is essential for fetching the correct instruction at the right time.
  - ALU Operand Selection: Mux decide which data should be sent to the ALU for computation, depending on the operation being performed.
  - Write-Back to Register: After an operation is completed, mux determines whether the result should be written back to a register or memory location.
- VIII. **Adders:** Used in some locations
  - PC (Program Counter): increment PC by 4 to take next instruction.
  - PC(Target): determine if there is Jump operation to give which instruction should be executed.

## RISC-V (Single Cycle)

Table 1 EXTENSION Table

ImmSrc	ImmExt	Type	Description
00	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed immediate
01	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed immediate
10	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	B	13-bit signed immediate
11	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed immediate

### Control Unit Structure:

 


Figure 4 Control Unit Block diagram

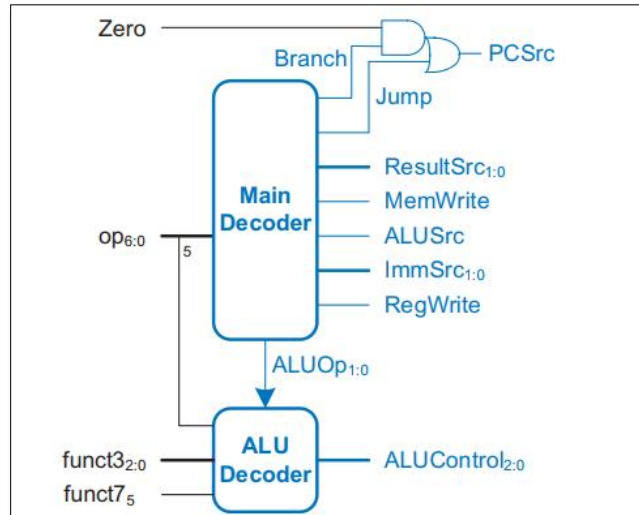


Figure 3 Control Unit Structure

Control Unit role:

- I. it takes the instruction from Datapath and put it in some of decoders to determine the control signals. I will explain more and show the table of each decoder.
- II. Control unit consist of two main Decoders
  - ALU Decoder: it determines ALUControl which specify which operation will run in ALU Block, Table 2 show the decoder operations.
  - Main Decoder: it determines rest of control signals which determine rest of operations, Table 3 show the main decoder operations.

## RISC-V (Single Cycle)

Table 2 ALU Decoder

ALUOp	funct3	{op <sub>5</sub> , funct7 <sub>5</sub> }	ALUControl	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt
	110	x	011 (or)	or
	111	x	010 (and)	and

Table 3 Main Decoder

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	00	1	0	01	0	00	0
sw	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	00	0	10	0
beq	1100011	0	10	0	0	xx	1	01	0
I-type ALU	0010011	1	00	1	0	00	0	10	0
jal	1101111	1	11	x	0	10	0	xx	1

## RISC-V (Single Cycle)

### III. Simulation:

#### ❖ Assembly code.

#	RISC-V Assembly	Description	Address	Machine Code
main:	addi x2, x0, 5	# x2 = 5	0	00500113
	addi x3, x0, 12	# x3 = 12	4	00C00193
	addi x7, x3, -9	# x7 = (12 - 9) = 3	8	FF718393
	or x4, x7, x2	# x4 = (3 OR 5) = 7	C	0023E233
	and x5, x3, x4	# x5 = (12 AND 7) = 4	10	0041F2B3
	add x5, x5, x4	# x5 = 4 + 7 = 11	14	004282B3
	beq x5, x7, end	# shouldn't be taken	18	02728863
	slt x4, x3, x4	# x4 = (12 < 7) = 0	1C	0041A233
	beq x4, x0, around	# should be taken	20	00020463
	addi x5, x0, 0	# shouldn't execute	24	00000293
around:	slt x4, x7, x2	# x4 = (3 < 5) = 1	28	0023A233
	add x7, x4, x5	# x7 = (1 + 11) = 12	2C	005203B3
	sub x7, x7, x2	# x7 = (12 - 5) = 7	30	402383B3
	sw x7, 84(x3)	# [96] = 7	34	0471AA23
	lw x2, 96(x0)	# x2 = [96] = 7	38	06002103
	add x9, x2, x5	# x9 = (7 + 11) = 18	3C	005104B3
	jal x3, end	# jump to end, x3 = 0x44	40	008001EF
	addi x2, x0, 1	# shouldn't execute	44	00100113
end:	add x2, x2, x9	# x2 = (7 + 18) = 25	48	00910133
	sw x2, 0x20(x3)	# [100] = 25	4C	0221A023
done:	beq x2, x2, done	# infinite loop	50	00210063

Figure 5 assembly code and its machine code (Taken from pdf of Harris for RISC-v)

#### ❖ Results:

main:	addi x2, x0, 5	# x2 = 5	0	00500113
	addi x3, x0, 12	# x3 = 12	4	00C00193
	addi x7, x3, -9	# x7 = (12 - 9) = 3	8	FF718393
	or x4, x7, x2	# x4 = (3 OR 5) = 7	C	0023E233
	and x5, x3, x4	# x5 = (12 AND 7) = 4	10	0041F2B3

00000000	00000000000000000000000000000000
00000001	00000000000000000000000000000000
00000002	00000000000000000000000000000101
00000003	000000000000000000000000000001100
00000004	00000000000000000000000000000111
00000005	00000000000000000000000000000100
00000006	000000000000000000000000000000000
00000007	000000000000000000000000000000011

	beq x5, x7, end	# shouldn't be taken	18	02728863
	slt x4, x3, x4	# x4 = (12 < 7) = 0	1C	0041A233
	beq x4, x0, around	# should be taken	20	00020463
	addi x5, x0, 0	# shouldn't execute	24	00000293
around:	slt x4, x7, x2	# x4 = (3 < 5) = 1	28	0023A233
	add x7, x4, x5	# x7 = (1 + 11) = 12	2C	005203B3

## RISC-V (Single Cycle)

00000000	00000000000000000000000000000000
00000001	00000000000000000000000000000000
00000002	00000000000000000000000000000101
00000003	000000000000000000000000000001100
00000004	000000000000000000000000000000001
00000005	000000000000000000000000000001011
00000006	00000000000000000000000000000000
00000007	000000000000000000000000000001100

- At the end of all instructions

0000005b	00000000000000000000000000000000
0000005c	00000000000000000000000000000000
0000005d	00000000000000000000000000000000
0000005e	00000000000000000000000000000000
0000005f	00000000000000000000000000000111
00000060	00000000000000000000000000000000
00000061	00000000000000000000000000000000
00000062	00000000000000000000000000000000
00000063	00000000000000000000000000000000
00000064	0000000000000000000000000000011001
00000065	00000000000000000000000000000000
00000066	00000000000000000000000000000000
00000067	00000000000000000000000000000000
00000068	00000000000000000000000000000000